



Figure 2 Beginning with a dc/dc converter, the circuit in Figure 1 switches on three additional converters in sequence and generates a POK signal. Pulling the circuit's on/off input low removes the POK signal and switches off all four converters in reverse order.