



**NOTES:**  
 $V_{OUT} = 2(1 + R/R_G)(V_1 - V_2)$ .  
 IC<sub>1</sub> IS AN OPA2111.

**Figure 1** You can build an instrumentation amplifier by providing a common feedback path for the two sides of a dual op amp.