



Figure 1 A single transistor, Q_1 , implements a switching regulator's slow-start-up feature, but its base current introduces a timing error.