



Figure 3 The dark-green trace shows that the circuit of Figure 2 produces the expected 1-second slow-start time interval, and the light-green trace illustrates Figure 1's too-brief start-up time. (The 1τ measurement equals 1 second.)