



NOTES:
 RS DESIGNATES A RADIO SHACK PART NUMBER.
 S₁ AND S₂ ARE NORMALLY HELD CLOSED BY THEIR RESPECTIVE MAGNETS.

Figure 1 This circuit protects the contents of a laboratory freezer or refrigerator by sounding an alarm when a door opens.