



Figure 1 A generic buck converter, IC<sub>1</sub>, provides constant-current drive for a high-brightness LED.