



Figure 2 An op amp, IC_2 , increases the LED-current error signal and reduces power dissipation in the sense resistor.