



Figure 11 The circuit of Figure 9 adapts to the isolated true-rms measurement of the current in a quartz crystal. The current probe's 50Ω impedance allows the elimination of the FET-input buffer and direct connection to IC₁. The current probe does not appreciably load the crystal in this oscillator test circuit.