



Figure 4 This ac/dc converter is typical of SCR-based designs. Feedback directs the SCR, which synchronizes with the ac line. The SCR's trigger-phase modulation controls the dc output.