



Figure 6 Optoisolators provide a safe, low-voltage digital output for this wideband-rms-measurement circuit. T<sub>1</sub> and associated circuitry provide isolated power for the rms converter, and a resistive divider performs high-voltage ac sensing. An ADC provides a serial output to the optoisolators. The accuracy of this circuit is 1% over a 200-kHz bandwidth.