



Figure 7 This ac-line-voltage regulator introduces no waveform distortion. IC₂ senses the rms value of line voltage and compares it with a reference. IC₂ then biases the photovoltaic optocoupler through Q₁. Q₂ sets the diode bridge's conductivity and closes the control loop. The input voltage must be 2V higher than the output voltage to maintain regulation.