



Figure 1 An external analog switch and a 555 timer provide a free-running oscillator with a fixed duty cycle.