



Figure 2 Add a potentiometer,  $R_4$ , to produce an output pulse that has a manually variable duty cycle.