



Figure 1 In this basic panoramic-potentiometer circuit, the position of  $R_7$ 's wiper controls the position of a monaural image in a stereo audio signal.