



Figure 3 Adding resistors R_7 and R_8 and SPST switch S_1 simplifies wiring and minimizes transients.