



Figure 1 Two transistors and an easily assembled transformer drive a white LED from a single 1.5V battery.