



Figure 1 In an H-bridge output-driver stage, diagonally opposed transistor pairs conduct to energize a dc motor. The circuit requires four control signals.