



Figure 1 On the rising edge of the output stage, such as at $T=T_x$, the low-side FET can briefly turn on due to a charge that couples through C_{GD} , which degrades the output stage's performance.