



Figure 1 An inductance-test oscillator comprises two transistors and a few passive components. (Editor's note: For best results, minimize the lengths of all components' leads.)