



Figure 1 A conventional 1-MΩ transimpedance amplifier exhibits 130 nV/√Hz of output noise, even with a noiseless op amp. Cooling the resistor reduces the noise, but can you do better without cooling?