



Figure 1 Amplifier  $A_1$  amplifies and inverts the common-mode voltage by a factor of  $-10$ . Then, the circuit applies this signal to an array of passive summation networks. An analog multiplexer selects the desired input signal, and op amp  $A_2$  supplies a compensating gain.