



NOTE: D₁ AND D₂ ARE HSMS-282Ls OR HSMS-282Cs.

Figure 1 Comparator IC₂ produces an output that switches state at the positive and the negative peaks of the input-voltage waveform.