



Figure 1 This circuit for a USB temperature sensor works in default UART and bit-bang modes.