



Figure 1 This circuit breaker provides both overvoltage and overcurrent protection. Other than the current flowing in R_3 , R_4 , and D_2 's cathode, the circuit draws no current from the supply in its normal untripped state.