



Figure 1 Use this circuit when your application requires zero drift and low output noise.