



**NOTE:**  $Q_R$  CAN BE AN OPTOCOUPLER OUTPUT OR A MANUAL SWITCH.

**Figure 1** Adding transistor  $Q_R$  to the L pin of a Topswitch switching power controller enables an on/off-control feature.