



Figure 1 This output-protection circuit provides continuous protection against overvoltage faults.