



Figure 1 Be sure to use a series resistor when connecting logic outputs to a transistor. Large FETs with substantial input capacitance may also need a series resistor to protect the logic-output stage. The resistor slows FET switching, but the resistive damping stabilizes the circuit.
