



Figure 2 CMOS-family logic, such as CD4000 and 74HCxxx, can have connected outputs because MOSFETS share current. Bipolar-logic families would need low-value resistors in each output leg to prevent current from hogging the bipolar-output stages.