



Figure 4 This miniature, 1A, LED-driver circuit operates on 8 to 50V and drives as many as three LEDs in series.