



Figure 1 The AD8034 sums the analyzer's reference output and a dc bias, supplying the negative-supply voltage for the device under test to perform negative-PSRR analysis.