



Figure 1 The serial dual DAC in this circuit gets an offset voltage from the microprocessor (not shown) during a power-on-calibration routine.