



Figure 1 Comprising off-the-shelf components, this circuit cascades two stages of boost to drive a string of 20 to 30 LEDs.