



BY BONNIE BAKER

# Outputs don't swing rail to rail

Single-supply amplifiers do not truly swing rail to rail at the output. Near the rail, the amplifier is nonlinear. For linear operation, the output of single-supply amplifiers can come within only 50 to 300 mV of each rail (Figure 1).

Single-supply-amplifier, rail-to-rail-output ads can give a false sense of security. Figure 1 shows a typical single-supply amplifier's output swing as you drive the output to the rails. The amplifier's linearity starts to degrade long before reaching the output-

swing maximums, and the amplifier output never reaches either rail.

The conditions of the dc-open-loop-gain specification define the amplifier's linear operating output range. The dc open loop gain in decibels is  $20 \log(\Delta V_{OUT}/\Delta V_{OS})$ , where  $V_{OUT}$  is the output voltage and  $V_{OS}$  is the input offset voltage. When you drive the output high,  $V_H$  is the maximum voltage level at the output in the dc-open-loop-gain measurement.  $V_{OH}$  is the absolute maximum voltage level with respect to  $V_{DD}$  (drain-to-drain voltage) that the output can reach.  $V_L$  is the minimum voltage level at the output in the dc-open-loop-gain measurement, and  $V_{OL}$  is the absolute minimum voltage level that the output can reach.  $V_H$  is less than  $V_{OH}$ , and  $V_L$  is greater than  $V_{OL}$ .

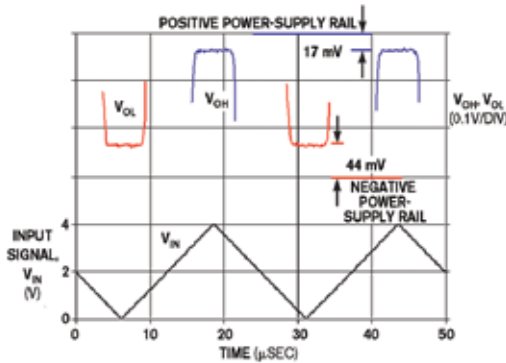


Figure 1 The lower plot illustrates the amplifier's input-voltage swing at a gain of 2V/V. The upper plot shows the amplifier's magnified output voltage.

From a signal-chain perspective, you can see an op amp's output limitations to swinging rail to rail when the op amp is driving an ADC. The FFT plot in Figure 2a shows the amplifier/ADC-combination response to a 1-kHz signal in a 5V system. The amplifier's typical closed-loop bandwidth is about 3 MHz with a typical slew rate of 2.3V/μsec. The amplifier output voltage swings from 140 mV to 4.66V. In this 5V-supply system, the headroom between the signal and rails is 140 mV. For this amplifier, the  $V_{OL}$  minimum specification is 15 mV above ground. The  $V_{OH}$  maximum specification is  $V_{DD} - 20$  mV.

Figure 2a illustrates the nonlinearity-output-stage effects with a single-supply CMOS amplifier by showing distortion at 2, 3, and 4 kHz and so on. By reducing the amplifier's output signal to 272 mV from each rail, the data looks perfect with only the ADC distortion (Figure 2b).

When using a single-supply amplifier, read the fine print! Some single-supply amps have output-stage charge pumps, allowing the amplifier's output swing to go to and well beyond the power-supply rails. In every case, read your data sheet and refer to the conditions on the open-loop-gain test. EDN

Bonnie Baker is a senior applications engineer at Texas Instruments. You can reach her at [bonnie@ti.com](mailto:bonnie@ti.com).

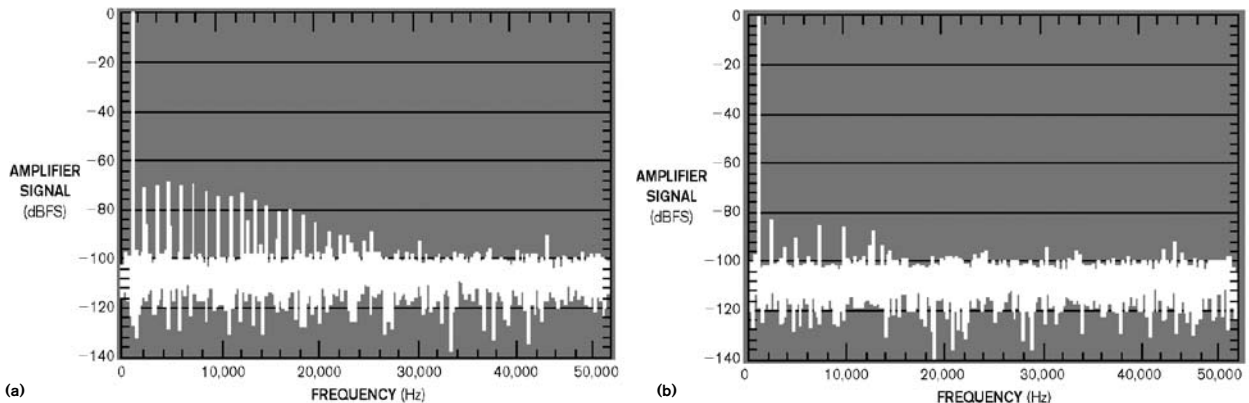


Figure 2 This 12-bit successive-approximation-register converter's maximum sampling speed is 100k samples/sec (a). Reducing the amp's output signal to 272 mV produces better results (b).