



Figure 1 A programmable, nonvolatile digital potentiometer functions as a simple AND gate. Setting the wiper to the device's highest value allows the input signal to propagate to the output; setting the wiper to the lowest value blocks the input signal.