



Figure 1 In this circuit, transistors Q_1 and Q_2 form a flip-flop that toggles at 60 kHz, providing a drive current for the output LED down to the 1V battery voltage.