



**Figure 1** With the four-wire touchscreen panel, the two active areas of the resistive touchscreen sense the X and Y pressure points (a). The equivalent circuit is simply a voltage divider (b).