



**Figure 1** This op-amp integrator ramps up or down at a preset rate, holding a final value equal to the input-voltage dc level.