



Figure 1 The conventional way to provide overvoltage protection is to add series resistors with the output node along with the clamping diodes to power-supply rails or other threshold voltages.