



Figure 2 This circuit works as a bipolar-current source when the voltage drop across source resistor R_6 becomes larger than the gate-threshold voltage of depletion-mode MOSFETs Q_1 and Q_2 , thus limiting the current through clamping diodes.