



Figure 4 This circuit requires only a couple of external components to use an SSR for output-overvoltage protection.