



NOTE: ASSUME A SOURCE RESISTANCE OF 0Ω .

Figure 1 If you vary the number of channels in this circuit, the current-feedback amp will help keep the closed-loop bandwidth constant.