



Figure A Current-feedback amplifiers find use in applications requiring high slew rates. The “tail” current of an input-differential pair does not limit the slew rate.