



Figure 1 This simple circuit clamps input-ac voltages higher than 260V rms to levels safe for the operation of the power MOSFET in a switched-mode power supply.