



Figure 1 The unique architecture of the AD8553 instrumentation amplifier, incorporating an input-voltage-to-current converter, allows 50% noise reduction with fewer components.