



Figure 1 A simple 13.56-MHz oscillator energizes an antenna coil, broadcasting power to the receiving circuit in Figure 2.