



Figure 2 This receiver rectifies the signal from the oscillator in Figure 1, powering low-current consumer gadgets.