



Figure 4 The bandwidth-versus-gain relationship demonstrates that, at low gains, there is significant loss of closed-loop bandwidth for the inverting amplifier.

---