

TABLE 5 GAIN VERSUS BETA AND BANDWIDTH

Inverting amplifier			Noninverting amplifier		
Gain	Beta	Bandwidth	Gain	Beta	Bandwidth
-1	0.500	0.500	1	1.000	1.000
-2	0.333	0.333	2	0.500	0.500
-3	0.250	0.250	3	0.333	0.333
-4	0.200	0.200	4	0.250	0.250
-5	0.167	0.167	5	0.200	0.200
-6	0.143	0.143	6	0.167	0.167
-7	0.125	0.125	7	0.143	0.143
-8	0.111	0.111	8	0.125	0.125
-9	0.100	0.100	9	0.111	0.111
-10	0.091	0.091	10	0.100	0.100