



Figure 4 The input pins of this op amp have series resistors and large capacitive-clamp diodes to protect it from ESD. An added benefit is that the part is more immune to RFI (courtesy Maxim Integrated Products).

---